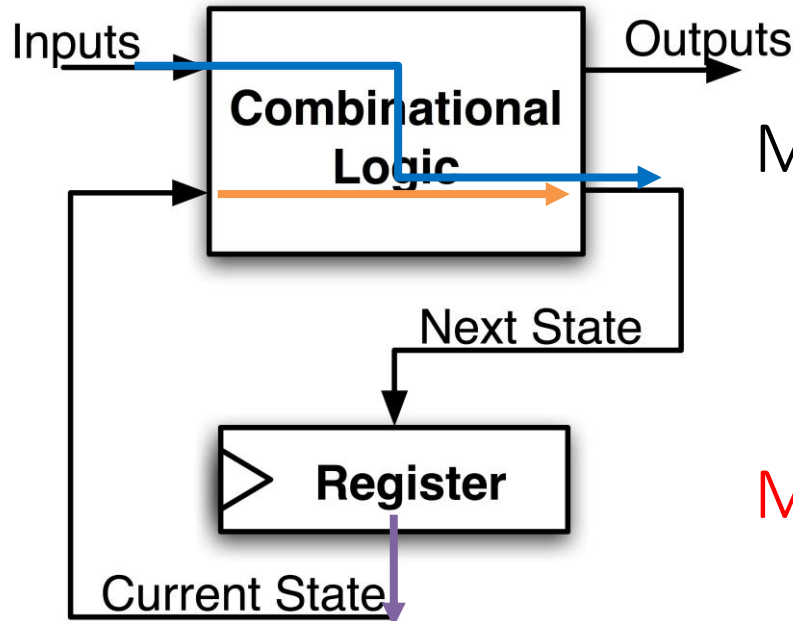


When Can the Input Change?

- ❖ When a register input changes shouldn't violate hold time (t_{hold}) or setup time (t_{setup}) constraints within a clock period (t_{period})
- ❖ Let $t_{input,i}$ be the time it takes for the input of a register to change for the i -th time in a single clock cycle, measured from the CLK trigger:
 - Then we need $t_{hold} \leq t_{input,i} \leq t_{period} - t_{setup}$ for all i
 - Two separate constraints!

Minimum Delay

- ❖ If shortest path to register input is too short, might violate hold time constraint
 - Input could change before state is “locked in”
 - Particularly problematic with *asynchronous* signals




$$\text{Min Delay} = \min(\text{CLK-to-Q Delay} + \text{Min CL Delay}, \text{Min CL Delay})$$

$$\text{Min Delay} \geq \text{Hold Time}$$

Maximum Clock Frequency

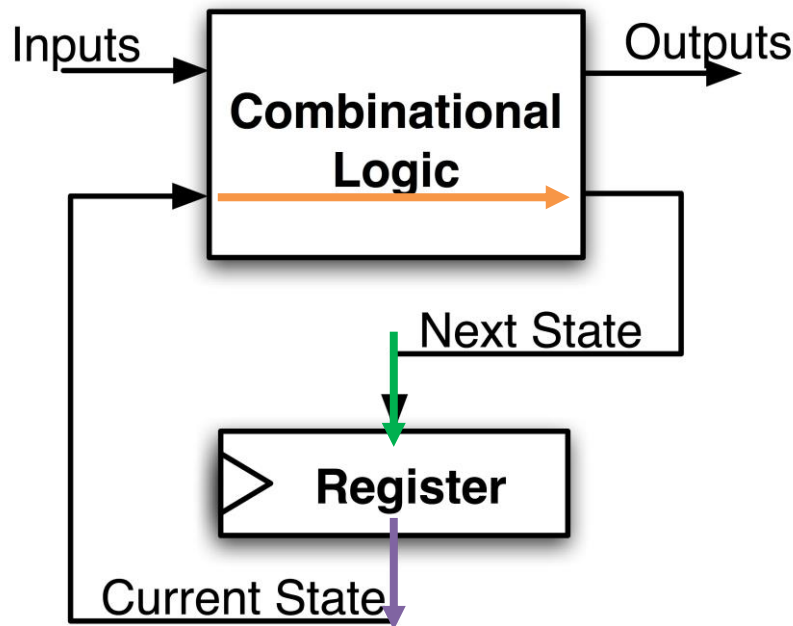- ❖ What is the max frequency of this circuit?
 - Limited by how much time needed to get correct Next State to Register (t_{setup} constraint)




$$\text{Max Delay} = \text{CLK-to-Q Delay} + \text{Max CL Delay} + \text{Setup Time}$$

$$\text{Min Period} = \text{Max Delay}$$
$$\text{Max Freq} = 1/\text{Min Period}$$

The Critical Path

 - ❖ The *critical path* is the longest delay between *any* two registers in a circuit
- ❖ The clock period must be *longer* than this critical path, or the signal will not propagate properly to that next register




Critical Path =

CLK-to-Q Delay
+ CL Delay 1
+ CL Delay 2
+ CL Delay 3
+ Adder Delay
+ Setup Time

Practice Question

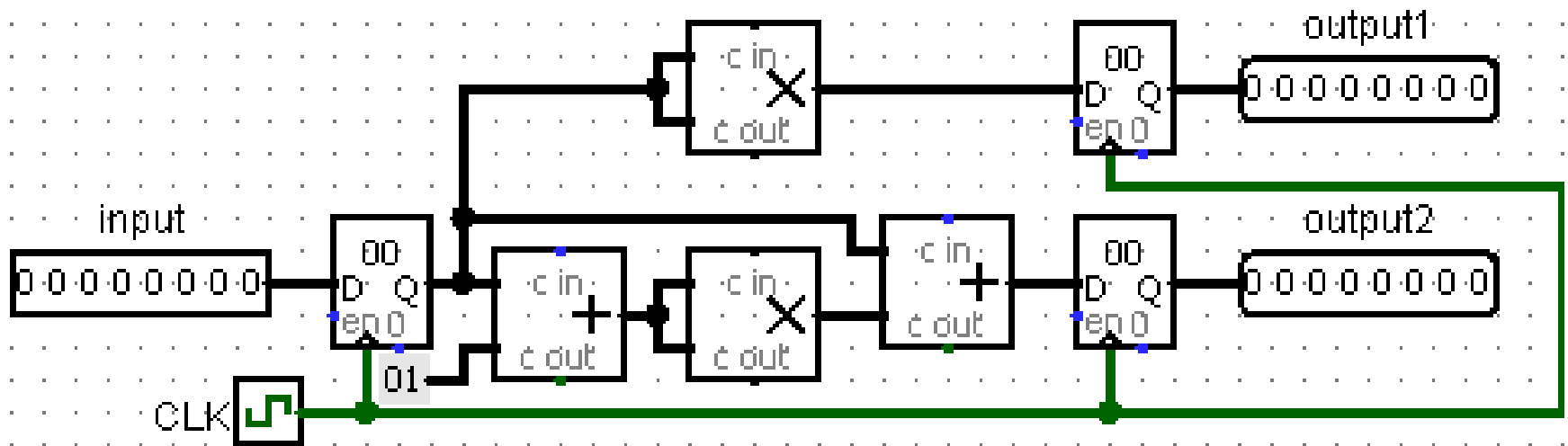
- ❖ We want to run on 1 GHz processor. $t_{\text{add}} = 100$ ps.
 $t_{\text{mult}} = 200$ ps. $t_{\text{setup}} = t_{\text{hold}} = 50$ ps. What is the
maximum $t_{\text{clk-to-q}}$ we can use?



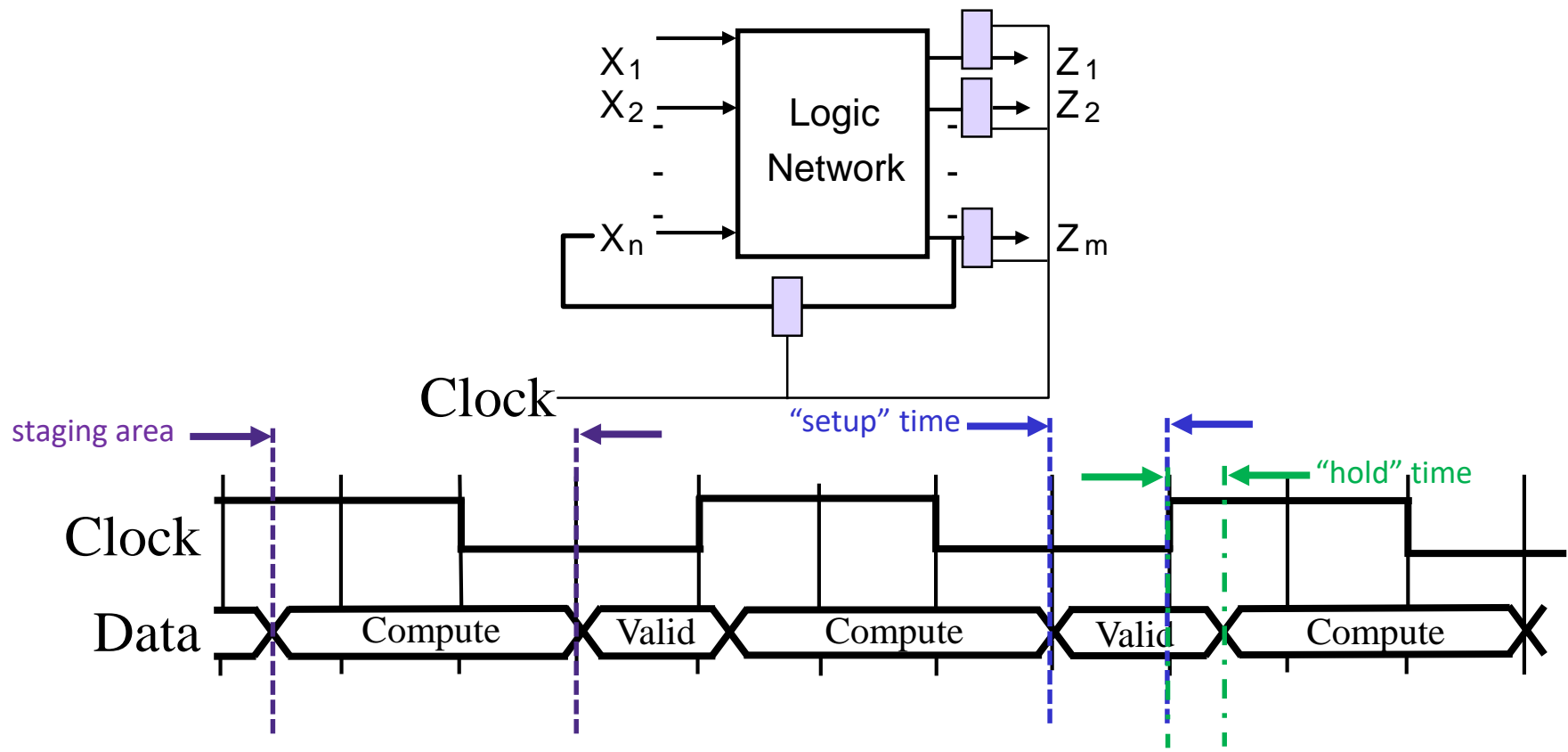(A) 550 ps (B) 750 ps (C) 500 ps (D) 700 ps


Safe Sequential Circuits

- ❖ Clocked elements on feedback, perhaps outputs
 - Clock signal synchronizes operation
 - Clocked elements hide glitches/hazards



Autopilot Revisited

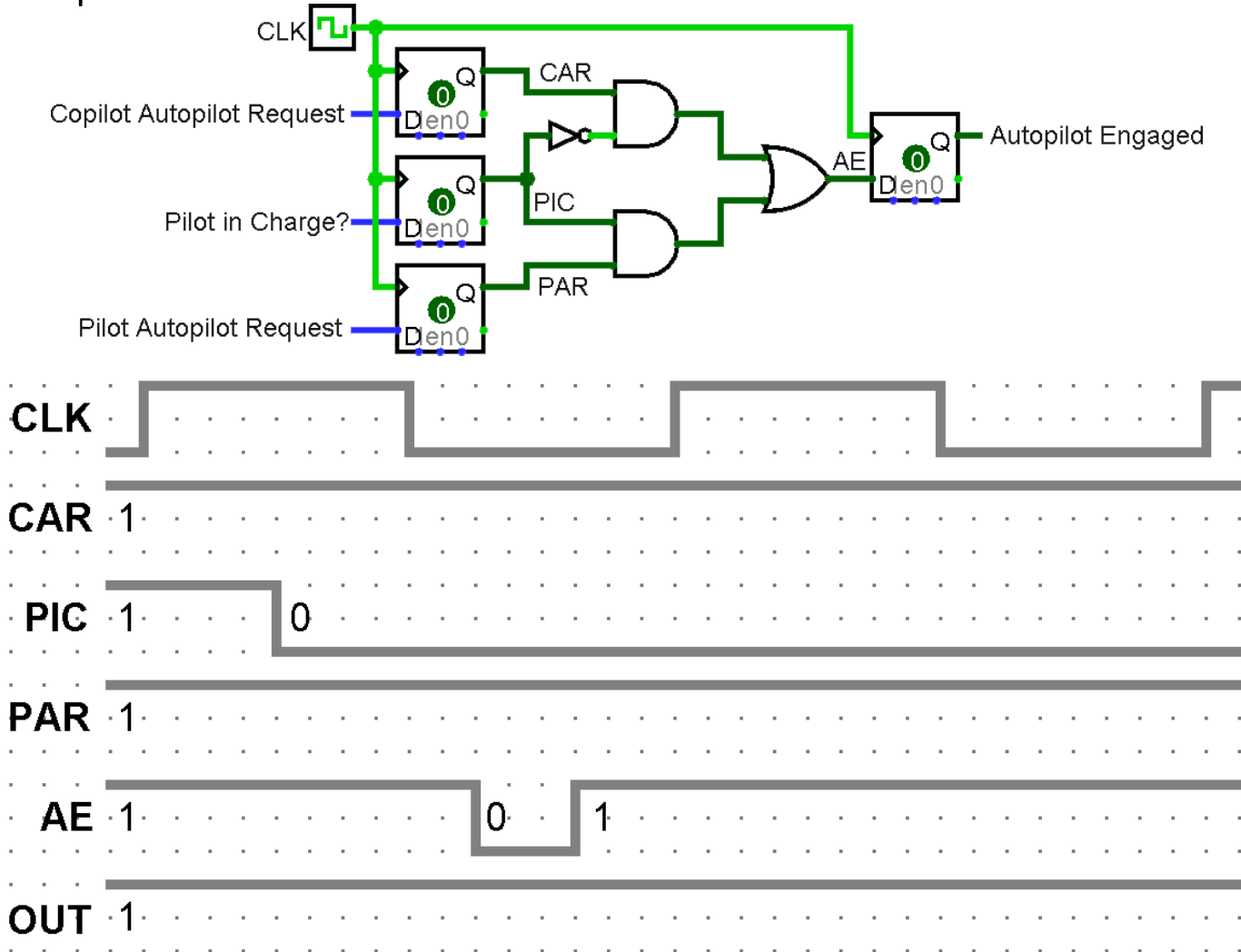- ❖ Flip-flops can “filter out” unintended behavior:





Waveform Diagrams Revisited

- ❖ Easiest to start with CLK on top
 - Solve signal by signal, from inputs to outputs
 - Can only draw the waveform for a signal if *all* of its input waveforms are drawn
- ❖ When does a signal update?
 - A *state element* updates based on CLK triggers
 - A *combinational element* updates ANY time ANY of its inputs changes

  
Example: SDS Waveform Diagram

- ❖ Assume: $t_{C2Q} = 3$ ticks, $t_{XOR} = 2$ ticks, $t_{NOT} = 1$ tick; $t_s = t_h = 0$
 - Note: clocking the gate is a *terrible* idea




Verilog: Basic D Flip-Flop, Register
 
```
module basic_D_FF (q, d, clk);  
    output logic q; // q is state-holding  
    input  logic d, clk;  
  
    always_ff @(posedge clk)  
        q <= d; // use <= for clocked elements  
endmodule
```


 
```
module basic_reg (q, d, clk);  
    output logic [7:0] q;  
    input  logic [7:0] d;  
    input  logic      clk;  
  
    always_ff @(posedge clk)  
        q <= d;  
endmodule
```





Procedural Blocks

- ❖ `always`: loop to execute over and over again
 - Block gets triggered by a *sensitivity list*
 - Any object that is assigned a value in an `always` statement must be declared as a variable (`logic` or `reg`).
 - Example:
 - **`always @ (posedge clk)`**
- ❖ `always_ff`: special SystemVerilog for SL
 - *Only for use with sequential logic – signal intent that you want flip-flops*
 - Example:
 - **`always_ff @ (posedge clk)`**

Blocking vs. Nonblocking

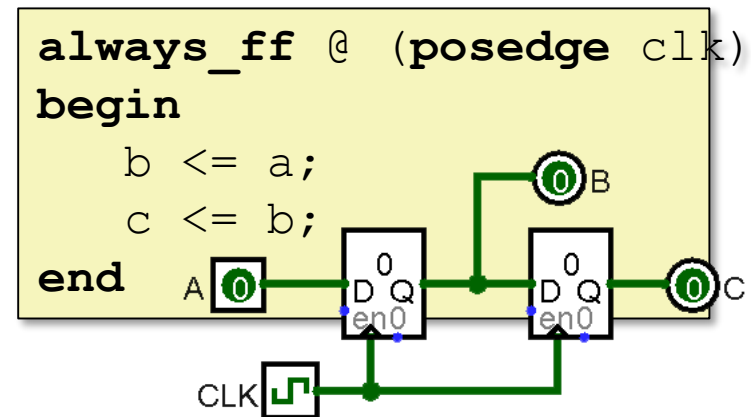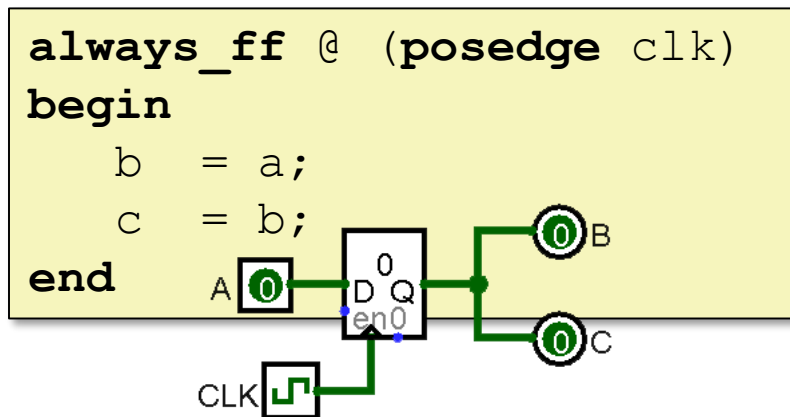- ❖ **Blocking** statement (`=`): statements executed sequentially
 - Resembles programming languages
- ❖ **Nonblocking** statement (`<=`): statements executed “in parallel”
 - Resembles hardware
- ❖ Example:




Verilog Coding Guidelines

 - 1) When modeling sequential logic, use *nonblocking* assignments
- 2) When modeling combinational logic with an `always_comb` block or assign statements, use *blocking* assignments
- 3) Avoid complex logic in `always_ff` blocks – instead, compute complex logic in `always_comb` blocks.
- 4) Do not mix *blocking* and *nonblocking* assignments in the same `always` block
- 5) Do not make assignments to the same variable from more than one `always` block

Verilog: D Flip-Flop w/Synchronous Reset

```
module D_FF (q, d, reset, clk);  
    output logic q; // q is state-holding  
    input  logic d, reset, clk;  
  
    always_ff @(posedge clk)  
        if (reset)  
            q <= 0;           // on reset, set to 0  
        else  
            q <= d;           // otherwise pass d to q  
  
endmodule
```



Verilog: Simulated Clock

- ❖ For simulation, you need to generate a clock signal:
 - For entirety of simulation/program, so use `always` block

Explicit
Edges:

```
initial
    clk = 0;
always begin
    #50  clk <= 1;
    #50  clk <= 0;
end
```

Toggle:

```
initial
    clk = 0;
always
    #50  clk <= ~clk;
```

- ❖ Define clock period:
 - Define **parameter**

```
parameter period = 100;
initial
    clk = 0;
always
    #(period/2)  clk <= ~clk;
```

Verilog Testbench with Clock

```
module D_FF_testbench;
    logic CLK, reset, d;
    logic q;

    parameter PERIOD = 100;

    D_FF dut (.q, .d, .reset, .CLK); // Instantiate the D_FF


    initial CLK <= 0; // Set up clock
    always #(PERIOD/2) CLK<= ~CLK;

    initial begin // Set up signals
        d <= 0; reset <= 1;
        @(posedge CLK); reset <= 0;
        @(posedge CLK); d <= 1;
        @(posedge CLK); d <= 0;
        @(posedge CLK); #(PERIOD/4) d <= 1;
        @(posedge CLK);
        $stop(); // end the simulation
    end
endmodule
```


Timing Controls

- ❖ Delay: `#<time>`
 - Delays by a specific amount of simulation time
 - Can do calculations in `<time>`
 - Examples: `# (PERIOD/4)`, `#50`
- ❖ Edge-sensitive: `@ (<pos/negedge> signal)`
 - Delays next statement until specified transition on signal
 - Example: `@ (posedge CLK)`
- ❖ Level-sensitive Event: `wait (<expression>)`
 - Delays next statement until `<expression>` evaluates to TRUE
 - Example: `wait (enable == 1)`

ModelSim Waveforms

 

```
initial begin
    d <= 0; reset <= 1;
    @ (posedge CLK) ;      reset <= 0;
    @ (posedge CLK) ; d <= 1;
    @ (posedge CLK) ; d <= 0;
    @ (posedge CLK) ; # (PERIOD/4) d <= 1;
    @ (posedge CLK) ;
    $stop();
end
```

Summary (1/2)

- ❖ State elements controlled by clock
 - Store information
 - Control the flow of information between other state elements and combinational logic
- ❖ Registers implemented from flip-flops
 - Triggered by CLK, pass input to output, can reset
- ❖ Critical path constrains clock rate
 - Timing constants: setup time, hold time, clk-to-q delay, propagation delays

Summary (2/2)

- ❖ Generating a clock
 - Manually create using `always` block
 - Need to decide on period
- ❖ Blocking vs. Non-blocking
 - Blocking: Statements executed “in series”
 - Non-blocking: Statements executed “in parallel”
 - Always use non-blocking for clocked elements
- ❖ Synchronous vs. Asynchronous
 - Whether signals are controlled by clock or not