

# FSM: Logic Simplification

PS	In	NS	Out
00	0	00	0
00	1	01	0
01	0	00	0
01	1	10	0
10	0	00	0
10	1	00	1
11	0	XX	X
11	1	XX	X

In \ PS				
	00	01	11	10
0				
1				

In \ PS				
	00	01	11	10
0				
1				

In \ PS				
	00	01	11	10
0				
1				

# FSM: Implementation


- ❖  $NS_1 = PS_0 \cdot In$
  - ❖  $NS_0 = \overline{PS_1} \cdot \overline{PS_0} \cdot In$
  - ❖  $Out = PS_1 \cdot In$
- 
- ❖ How do we test the FSM?
    - “Take” every *transition* that we care about!

# State Diagram Properties

- ❖ For  $S$  states, how many state bits do I use?
- ❖ For  $I$  inputs, what is the *maximum* number of transition arrows on the state diagram?
  - Can sometimes combine transition arrows
  - Can sometimes omit transitions (don't cares)
- ❖ For  $s$  state bits and  $I$  inputs, how big is the truth table?
 
# Vending Machine Example

- ❖ Vending machine description/behavior:
  - Single coin slot for dimes and nickels
  - Releases gumball after  $\geq 10$  cents deposited
  - Gives no change



- ❖ State Diagram:

# Vending Machine State Table

PS	N	D	NS	Open
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

PS,N		00	01	11	10
D	0				
	1				

PS,N		00	01	11	10
D	0				
	1				

# Vending Machine Implementation

# Outline

- ❖ Flip-Flop Realities
- ❖ Finite State Machines
- ❖ **FSMs in Verilog**

# FSMs in Verilog: Declarations

- ❖ Let's examine the components of the Verilog FSM example module on the next few slides

```
module simpleFSM (clk, reset, w, out);  
    input logic clk, reset, w;  
    output logic out;  
  
    logic [1:0] ps;    // Present State  
    logic [1:0] ns;    // Next State  
  
    ...
```



# FSMs in Verilog: Combinational Logic

```
// State Encodings - so you don't have to remember!
parameter [1:0] A = 2'b00, B = 2'b01, C = 2'b10;

// Next State Logic
always_comb
    case (ps)
        A: if (w)    ns = B;
           else      ns = A;
        B: if (w)    ns = C;
           else      ns = A;
        C: if (w)    ns = C;
           else      ns = A;
        default:     ns = 2'bxx;
    endcase

// Output Logic - could have been in "always" block
// or part of Next State Logic.
assign out = (ps == C);
```

# FSMs in Verilog: State

...

```
// Sequential Logic (DFFs)
always_ff @(posedge clk)
    if (reset)
        ps <= A;
    else
        ps <= ns;
```

```
endmodule
```

# Reminder: Blocking vs. Non-blocking

- ❖ NEVER mix in one always block!
- ❖ Each variable written in only one always block

❖ Blocking (=) in CL:

```
// Output logic
assign out = (ps == C);

// Next State Logic
always_comb
  case (ps)
    A: if (w) ns = B;
       else ns = A;
    B: if (w) ns = C;
       else ns = A;
    C: if (w) ns = C;
       else ns = A;
    default: ns = 2'bxx;
  endcase
```

❖ Non-blocking (<=) in SL:

```
// Sequential Logic
always_ff @(posedge clk) begin
  if (reset)
    ps <= A;
  else
    ps <= ns;
end
```

# One or Two Blocks?

- ❖ We showed the state update in two separate blocks:
  - `always_comb` block that calculates the next state (`ns`)
  - `always_ff` block that defines the register (`ps` updates to last `ns` on clock trigger)
- ❖ Can this be done with a single block?
  - If so, which one: `always_comb` or `always_ff`

# One or Two Blocks?

```
always_comb
  case (ps)
    A: if (w)   ns = B;
        else    ns = A;
    B: if (w)   ns = C;
        else    ns = A;
    C: if (w)   ns = C;
        else    ns = A;
    default:    ns = 2'bxx;
  endcase

always_ff @(posedge clk)
  if (reset)
    ps <= A;
  else
    ps <= ns;
```

```
always_ff @(posedge clk)
  if (reset)
    ps <= A;
  else
    case (ps)
      A: if (w)   ps <= B;
          else    ps <= A;
      B: if (w)   ps <= C;
          else    ps <= A;
      C: if (w)   ps <= C;
          else    ps <= A;
      default:    ps <= 2'bxx;
    endcase
```


# FSM Testbench (1/2)

```
module simpleFSM_testbench();  
    logic clk, reset, w;  
    logic out;  
  
    simpleFSM dut (.clk, .reset, .w, .out);  
  
    // Set up the clock  
    parameter CLOCK_PERIOD=100;  
  
    initial clk<=1;  
    always # (CLOCK_PERIOD/2) clk <= ~clk;  
  
    ...
```

# FSM Testbench (2/2)

```
// Set up the inputs to the design (each line is a clock cycle)
initial begin
    @(posedge clk); reset <= 1;
    @(posedge clk); reset <= 0; w <= 0;
    @(posedge clk);
    @(posedge clk);
    @(posedge clk);
    @(posedge clk); w <= 1;
    @(posedge clk); w <= 0;
    @(posedge clk); w <= 1;
    @(posedge clk);
    @(posedge clk);
    @(posedge clk);
    @(posedge clk); w <= 0;
    @(posedge clk);
    @(posedge clk);
    $stop; // End the simulation
end
endmodule
```

# Testbench Waveforms

 

- ❖ What is the min # of clock cycles to *completely* test this FSM?



# Summary

- ❖ Gating the clock and external inputs can cause timing issues and metastability
- ❖ FSMs visualize state-based computations
  - Implementations use registers for the state (PS) and combinational logic to compute the next state and output(s)
  - Mealy machines have outputs based on *state transitions*
- ❖ FSMs in Verilog usually have separate blocks for state updates and CL
  - Blocking assignments in CL, non-blocking assignments in SL
  - Testbenches need to be carefully designed to test all state transitions