

# Intro to Digital Design

## Combinational Logic


Instructor: Clarice Larson

### Data transfer system connects silicon chips with a hair's-width cable

“Researchers have developed a data transfer system that can transmit information 10 times faster than a USB. The new link pairs high-frequency silicon chips with a polymer cable as thin as a strand of hair. The system may one day boost energy efficiency in data centers and lighten the loads of electronics-rich spacecraft.”

“The researchers suggest “data-dense” applications, like server farms, could be early adopters of the new links, since they could dramatically cut data centers’ high energy demands. The link could also be a key solution for the aerospace and automotive industries, which place a premium on small, light devices ...”
 
<https://news.mit.edu/2021/data-transfer-system-silicon-0224>



# Lecture Outline

- ❖ Course Logistics
- ❖ Course Motivation
- ❖ Combinational Logic Review
- ❖ Combinational Logic in the Lab

# Course Staff

❖ Instructor: Clarice Larson

❖ TAs:



Hafsa



Laksh



Matthew



Noah



Sahar



Suliman

# Virtual Reality

- ❖ Zoom will be used for Lectures, Office Hours, Demos
- ❖ Students will not have access to CSE lab spaces
  - Install Quartus on your machine
- ❖ Kits can be picked up in person or shipped based on your preference (**Pre-Course Survey**)

# Course Information

- ❖ **Instructor:**Clarice Larson (clarice@cs.uw.edu)
- ❖ **TAs:**
  - Matthew Cinnamon (cinnam@cs.uw.edu)
  - Laksh Gupta (lg2000@cs.uw.edu)
  - Hafsa Khan (hafsa@cs.uw.edu)
  - Sahar Osman (saharo@cs.uw.edu)
  - Suliman Osman (osman92@cs.uw.edu)
  - Noah Ponto (ponton@cs.uw.edu)
- ❖ **Lab Hours:** Wed & Thu 2:30-5:20 pm (Zoom)
- ❖ **Canvas:** <https://canvas.uw.edu/courses/1448815>
- ❖ **Discussion:** <https://edstem.org/us/courses/4902/discussion/>

# Grading

## ❖ Labs (66%)

- 6 regular labs – 1 week each
  - Labs 2-3: 60 points each, Labs 1, 4-6: 100 points each
- 1 “final project” – 2 weeks
  - Lab 7 Check-In: 10 points, Lab 7: 150 points

## ❖ 3 Quizzes (no final exam)

- Quiz 1 (10%): 20 min in class on April 27
- Quiz 2 (10%): 25 min in class on May 18
- Quiz 3 (14%): 40 min in class on June 1

# Labs

- ❖ Labs are a combination of report + demo
  - Submit materials via Canvas **Wednesdays before 2:30 pm**
    - This is *before* your demo
  - 10-minute demos done in lab sections (Pre-course Survey)
- ❖ Each student will get a lab kit for the quarter
  - Install software on laptop (Windows or VM)
  - Lab sections are for access to TAs
- ❖ Penalties on lab submissions and demos:

<b>Lateness</b>	< 24 hr	< 48 hr	< 72 hr	$\geq$ 72 hr
<b>Penalty</b>	10%	30%	60%	100%


# Collaboration Policy

- ❖ Labs and final project are to be completed *individually*
  - Learn by doing
  - Violation of these rules is grounds for failing the class
- ❖ OK:
  - Discussing lectures and/or readings, studying together
  - *High-level* discussion of general approaches
  - Help with debugging, peculiarities with tools, etc.
- ❖ Not OK:
  - Developing a lab together
  - Giving away solutions or having someone else do your lab for you


 
# Course Workload

- ❖ The workload ramps up significantly towards the end of the quarter:




# Lecture Outline

- ❖ Course Logistics
- ❖ **Course Motivation**
- ❖ Combinational Logic Review
- ❖ Combinational Logic in the Lab

# Course Motivation

- ❖ Smaller, faster, cheaper hardware has enabled so many advances in electronics
  - Computers & phones
  - Vehicles (cars, planes)
  - Robots
  - Portable & household electronics
  
- ❖ An *introduction* to digital logic design
  - **Lecture:** How to think about hardware, basic higher-level circuit design techniques – preparation for EE/CSE469
  - **Lab:** Hands-on FPGA programming using Verilog – preparation for EE/CSE371

# Digital vs. Analog

 


## Digital:

Discrete set of possible values

## Binary (2 values):

On, 3.3 V, high, TRUE, "1"

Off, 0 V, low, FALSE, "0"

 

## Analog:

Values vary over a continuous range

# Digital vs. Analog Systems

- ❖ Digital systems are more reliable and less error-prone
  - Slight errors can cascade in Analog system
  - Digital systems reject a significant amount of error; easy to cascade
- ❖ Computers use digital circuits internally
  - CPU, memory, I/O
- ❖ Interface circuits with “real world” often analog
  - Sensors & actuators

*This course is about logic design,  
not system design (processor architecture),  
and not circuit design (transistor level)*

# Digital Design: What's It All About?

- ❖ Create an implementation using a set of building blocks given a functional description and constraints
- ❖ Digital design is in some ways more art than a science
  - The creative spirit is in combining primitive elements and other components in new ways to achieve a desired function
- ❖ However, unlike art, we have objective measures of a design (*i.e.* constraints):
  - Performance
  - Power
  - Cost

# Digital Design: What's It All About?

- ❖ How do we learn how to do this?
  - Learn about the building blocks and how to use them
  - Learn about design representations
  - Learn formal methods and tools to manipulate representations
  - Look at design examples
  - Use trial and error – CAD tools and prototyping (practice!)


# Lecture Outline

- ❖ Course Logistics
- ❖ Course Motivation
- ❖ **Combinational Logic Review**
- ❖ Combinational Logic in the Lab



# Combinational vs. Sequential Logic


## ❖ Combinational Logic (CL)

 

Network of logic gates without feedback.

Outputs are functions only of inputs.

## ❖ Sequential Logic (SL)

 

The presence of feedback introduces the notion of “state.”

Circuits that can “remember” or store information.

# Representations of Combinational Logic

- ❖ Text Description
- ❖ Circuit Description
  - ~~Transistors~~ Not covered in 369
  - Logic Gates
- ❖ Truth Table
- ❖ Boolean Expression
  
- ❖ *All are equivalent!*


# Example: Simple Car Electronics

- ❖ Door Ajar (DriverDoorOpen, PassengerDoorOpen)
- ❖ High Beam Indicator (LightsOn, HighBeamOn)
- ❖ Seat Belt Light (DriverBeltIn, PassengerBeltIn, Passenger)

# Truth Tables

- ❖ Table that relates the inputs to a combinational logic (CL) circuit to its output
  - Output *only* depends on current inputs
  - Use abstraction of 0/1 instead of high/low voltage
  - Shows output for *every* possible combination of inputs (“black box” approach)
  
- ❖ How big is the table?
  - 0 or 1 for each of  $N$  inputs
  - Each output is a separate function of inputs, so don't need to add rows for additional outputs

# CL General Form

 


If  $N$  inputs, how many distinct functions  $F$  do we have?

a	b	c	d	y
0	0	0	0	$F(0,0,0,0)$
0	0	0	1	$F(0,0,0,1)$
0	0	1	0	$F(0,0,1,0)$
0	0	1	1	$F(0,0,1,1)$
0	1	0	0	$F(0,1,0,0)$
0	1	0	1	$F(0,1,0,1)$
0	1	1	0	$F(0,1,1,0)$
1	1	1	1	$F(0,1,1,1)$
1	0	0	0	$F(1,0,0,0)$
1	0	0	1	$F(1,0,0,1)$
1	0	1	0	$F(1,0,1,0)$
1	0	1	1	$F(1,0,1,1)$
1	1	0	0	$F(1,1,0,0)$
1	1	0	1	$F(1,1,0,1)$
1	1	1	0	$F(1,1,1,0)$
1	1	1	1	$F(1,1,1,1)$

# Logic Gates (1/2)

- ❖ Special names and symbols:

NOT

 

A	Out
0	1
1	0

AND



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

# Logic Gates (2/2)

❖ Special names and symbols:

NAND



A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

NOR



A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

XOR



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0


# More Complicated Truth Tables

## 3-Input Majority

How many rows?

A	B	C	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

## 1-bit Adder

 

A	B	Carry	Sum
0	0		
0	1		
1	0		
1	1		



# Boolean Algebra

- ❖ Represent inputs and outputs as variables
  - Each variable can only take on the value 0 or 1
- ❖ Overbar is NOT: “logical complement”
  - If  $A$  is 0, then  $\bar{A}$  is 1 and vice-versa
- ❖ Plus (+) is 2-input OR: “logical sum”
- ❖ Product ( $\cdot$ ) is 2-input AND: “logical product”
- ❖ All other gates and logical expressions can be built from combinations of these
  - e.g.  $A \text{ XOR } B = A \oplus B = \bar{A}B + \bar{B}A$

# Truth Table to Boolean Expression

## ❖ Read off of table

- For 1, write variable name
- For 0, write complement of variable

a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

## ❖ *Sum of Products (SoP)*

- Take rows with 1's in output column, sum products of inputs
- $C = \bar{A}B + \bar{B}A$

We can show that these are equivalent!

## ❖ *Product of Sums (PoS)*

- Take rows with 0's in output column, product the sum of the complements of the inputs
- $C = (A + B) \cdot (\bar{A} + \bar{B})$

# Basic Boolean Identities

$$\diamond X + 0 = X$$

$$\diamond X \cdot 1 = X$$

$$\diamond X + 1 = 1$$

$$\diamond X \cdot 0 = 0$$

$$\diamond X + X = X$$

$$\diamond X \cdot X = X$$

$$\diamond X + \overline{X} = 1$$

$$\diamond X \cdot \overline{X} = 0$$

$$\diamond \overline{\overline{X}} = X$$

# Basic Boolean Algebra Laws

## ❖ Commutative Law:

$$X + Y = Y + X$$

$$X \cdot Y = Y \cdot X$$

## ❖ Associative Law:

$$X + (Y + Z) = (X + Y) + Z$$

$$X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

## ❖ Distributive Law:

$$X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

$$X + YZ = (X + Y) \cdot (X + Z)$$

# Advanced Laws (Absorption)

$$\diamond X + XY = X$$

$$\diamond XY + X\bar{Y} = X$$

$$\diamond X + \bar{X}Y = X + Y$$

$$\diamond X(X + Y) = X$$

$$\diamond (X + Y)(X + \bar{Y}) = X$$

$$\diamond X(\bar{X} + Y) = XY$$

# Practice Problem

❖ Boolean Function:  $F = \bar{X}YZ + XZ$

Truth Table:

X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Simplification:

# Technology Break

# Lecture Outline

- ❖ Course Logistics
- ❖ Course Motivation
- ❖ Combinational Logic Review
- ❖ **Combinational Logic in the Lab**



# Why Is This Useful?

- ❖ Logic minimization: reduce complexity at gate level
  - Allows us to build smaller and faster hardware
  - Care about both # of gates, # of literals (gate inputs), # of gate levels, and types of logic gates

# Why Is This Useful?

## ❖ Faster hardware?

- Fewer inputs implies faster gates in some technologies
- Fan-ins (# of gate inputs) are limited in some technologies
- Fewer levels of gates implies reduced signal propagation delays
- # of gates (or gate packages) influences manufacturing costs
- Simpler Boolean expressions → smaller transistor networks → smaller circuit delays → faster hardware
- Does the type of gate matter?

# Does the Type of Gate Matter?

❖ Yes!

2-Input Gate Type	# of transistors
NOT	2
AND	6
OR	6
NAND	4
NOR	4
XOR	8
XNOR	8

❖ Can recreate all other gates using only NAND or only NOR gates

- Called “universal” gates
- *e.g.*  $A \text{ NAND } A = \bar{A}$ ,  $B \text{ NOR } B = \bar{B}$
- DeMorgan’s Law helps us here!

# DeMorgan's Law

$$\diamond \overline{X + Y} = \bar{X} \cdot \bar{Y}$$

$$\diamond \overline{X \cdot Y} = \bar{X} + \bar{Y}$$


X	Y	$\bar{X}$	$\bar{Y}$	NOR		NAND	
				$\overline{X + Y}$	$\bar{X} \cdot \bar{Y}$	$\overline{X \cdot Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1		1	
0	1	1	0	0		1	
1	0	0	1	0		1	
1	1	0	0	0		0	

- ❖ In Boolean Algebra, converts between NAND/NOR and OR/AND expressions

- $Z = \overline{(A + B + \bar{C}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C})}$


- $Z = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$

 - At gate level, can convert from NAND/NOR to OR/AND gates
  - “Flip” all input/output bubbles and “switch” gate




# DeMorgan's Law Practice Problem

- ❖ Simplify the following diagram:

 

- ❖ Then implement with only NAND gates:

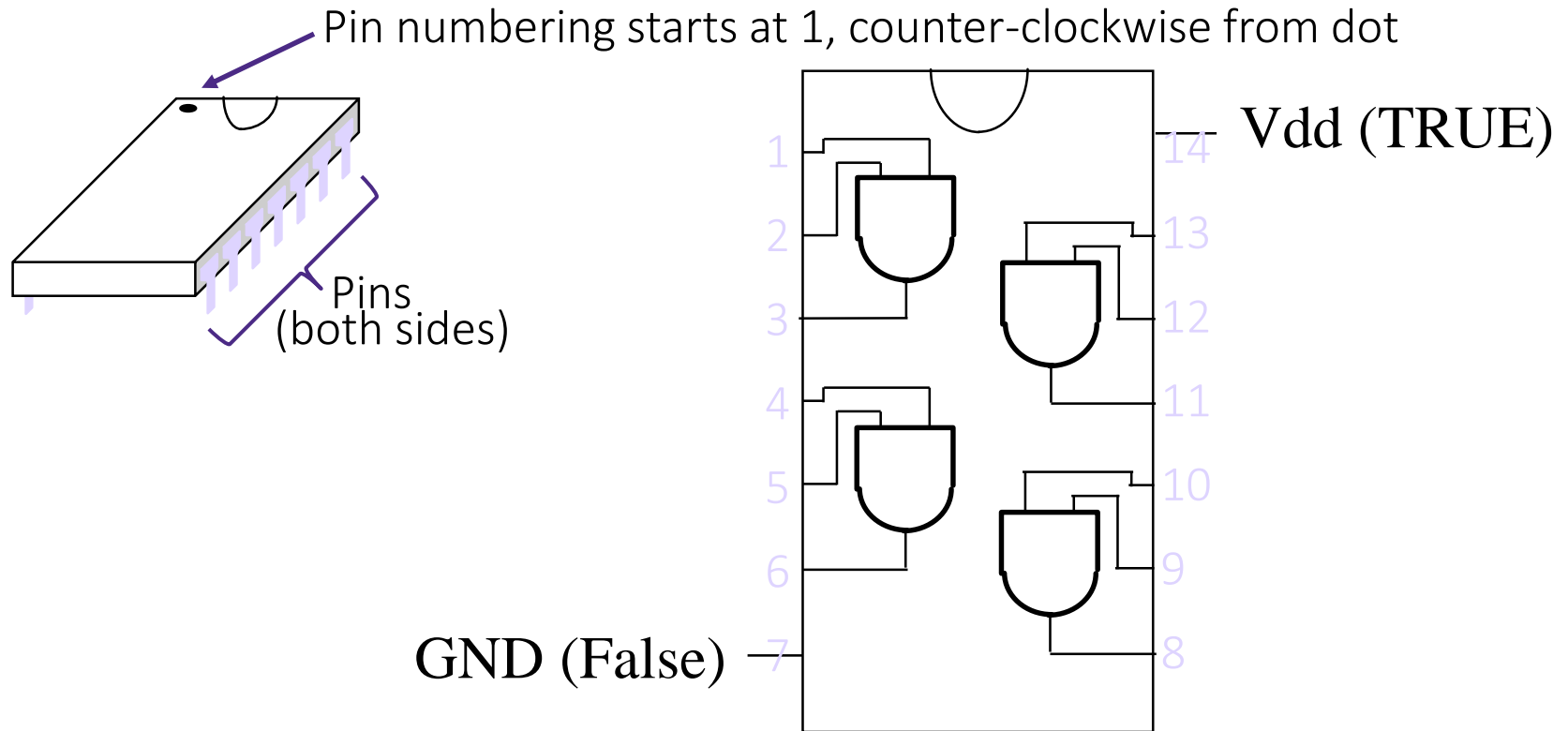
# Transistor-Transistor Logic (TTL) Packages




- ❖ Diagrams like these and other useful/helpful information can be found on part **data sheets**
  - It's really useful to learn how to read these
 
# Mapping truth tables to logic gates



- ❖ Given a truth table:
  - 1) Write the Boolean expression
  - 2) Minimize the Boolean expression
  - 3) Draw circuit diagram with gates
  - 4) Map to available gates
  - 5) Determine # of packages and their connections



(4) →

 

# Breadboarding circuits

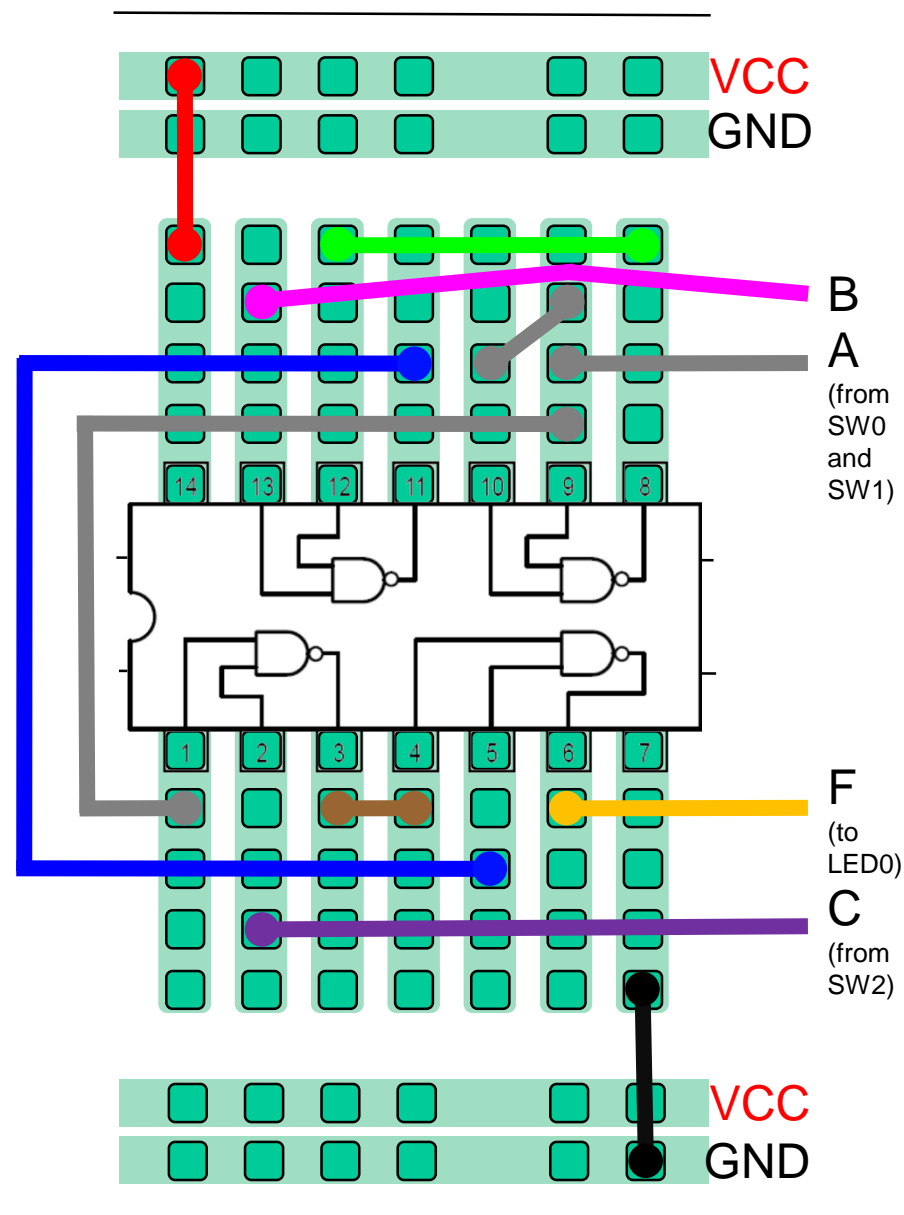 



# Summary

- ❖ Digital systems are constructed from Combinational and Sequential Logic
- ❖ Logic minimization to create smaller and faster hardware
- ❖ Gates come in TTL packages that require careful wiring

