 


Lecture Outline

- ❖ Karnaugh Maps (K-maps)
- ❖ Design Examples

Design Example: 2-bit Adder

❖ Block Diagram and Truth Table:



A	B	C	D	X	Y	Z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Design Example: 2-bit Adder

K-map for X

CD \ AB		A			
		0	0	0	0
C	0	0	0	1	0
	1	0	1	1	1
	0	0	1	1	1
	1	0	0	1	1
		B			
		D			

K-map for Y

CD \ AB		A			
		0	0	1	1
C	0	0	1	0	1
	1	1	0	1	0
	0	1	1	0	0
	1	0	0	1	0
		B			
		D			

K-map for Z

CD \ AB		A			
		0	1	1	0
C	0	1	0	0	1
	1	1	0	0	1
	0	1	1	0	0
	1	0	0	1	0
		B			
		D			

X =

Y =

Z =

Don't Cares

- ❖ Use symbol 'X' to mean it can be either a 0 or 1
 - Make choice to simplify final expression

	AB		A	
CD	0	0	X	0
	1	1	X	1
	1	1	0	0
	0	X	0	0
			B	
				D

Let all X = 0:

F =

CD \ AB		A			
		0	0	X	0
C	1	1	X	1	
	1	1	0	0	
	0	X	0	0	
	B				
		D			

Let all X = 1:

F =


	AB		A	
CD	0	0	X	0
	1	1	X	1
	1	1	0	0
	0	X	0	0
			B	
	C			D

Choose wisely:

F =

Design Example: Rock-Paper-Scissors

 
- ❖ Rock (00), Paper (01), Scissors (10) for two players P0 and P1
- ❖ **Output:** Win = Winner's ID (0/1)
Tie = 1 if Tie, 0 else



P1		P0		Win	Tie
A	B	C	D		
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		


Case Study: Seven-Segment Display

❖ Chip to drive digital display

 


B3	B2	B1	B0	Val
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9

Case Study: Seven-Segment Display

 


B3	B2	B1	B0	Val	L0	L1	L2	L3	L4	L5	L6
0	0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	0	1	1	0	0	0	0
0	0	1	0	2	1	1	0	1	1	0	1
0	0	1	1	3	1	1	1	1	0	0	1
0	1	0	0	4	0	1	1	0	0	1	1
0	1	0	1	5	1	0	1	1	0	1	1
0	1	1	0	6	1	0	1	1	1	1	1
0	1	1	1	7	1	1	1	0	0	0	0
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

 

Case Study: Seven-Segment Display

❖ Implement L5:

B3	B2	B1	B0	L5
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

 

7-Seg Display in Verilog

```
module seg7 (bcd, leds);  
    input  logic [3:0] bcd;  
    output logic [6:0] leds;  
  
    always_comb  
        case (bcd)  
            // 3210          6543210  
            4'b0000: leds = 7'b0111111;  
            4'b0001: leds = 7'b0000110;  
            4'b0010: leds = 7'b1011011;  
            4'b0011: leds = 7'b1001111;  
            4'b0100: leds = 7'b1100110;  
            4'b0101: leds = 7'b1101101;  
            4'b0110: leds = 7'b1111101;  
            4'b0111: leds = 7'b0000111;  
            4'b1000: leds = 7'b1111111;  
            4'b1001: leds = 7'b1101111;  
            default: leds = 7'bX;  
        endcase  
endmodule
```

Procedural Blocks

❖ `assign`: continuous assignment

■ *e.g.* **assign** `F = ~((A & B) | (C & D));`

❖ `initial`: executes once at time zero

■ Set initial values (**simulation only!!!**)

■ Define testbench waveforms (and `monitor`)

■ *e.g.* **initial begin**

for (`i=0; i<8; i=i+1`)

`{SEL, I, J} = i; #10;`


end

Procedural Blocks

- ❖ `always`: loop to execute over and over again
 - Block gets triggered by a *sensitivity list*
 - Any object that is assigned a value in an `always` statement must be declared as a variable (`logic`).
 - Examples:
 - **`always`** @ (a **or** b **or** c) ↔ `always` @ (a, b, c)
 - **`always`** @ (*) implicitly contains all read signals within the block
- ❖ `always_comb`: special SystemVerilog for CL
 - Similar to `always` @ (*), but generally more robust
 - *Only for use with combinational logic!!!*

Verilog: Extend 7-Seg to Hex

 - ❖ Show “A” on 0b1010 (ten) to “F” on 0b1111 (fifteen)



```
module seg7 (bcd, leds);  
    input logic [3:0] bcd;  
    output logic [6:0] leds;  
  
    always_comb  
        case (bcd)  
            // BCD[]          LEDS[]  
            // 3210          6543210  
            4'b0000: leds = 7'b0111111;  
            4'b0001: leds = 7'b00000110;  
            4'b0010: leds = 7'b1011011;  
            4'b0011: leds = 7'b1001111;  
            4'b0100: leds = 7'b1100110;  
            4'b0101: leds = 7'b1101101;  
            4'b0110: leds = 7'b1111101;  
            4'b0111: leds = 7'b00000111;  
            4'b1000: leds = 7'b1111111;  
            4'b1001: leds = 7'b1101111;  
            default: leds = 7'bX;  
        endcase  
endmodule
```

Circuit Implementation Techniques

- ❖ Truth Tables – “Black box” circuit description
- ❖ Boolean Algebra – Math form for optimization
 - *K-Maps* – Alternate simplification technique
- ❖ Circuit Diagrams
- ❖ Verilog – Simulation & mapping to FPGAs