



BAHRIA UNIVERSITY, (Karachi Campus)

Department of Software Engineering QUIZ - 3

COURSE TITLE: **Computer Architecture & Logic Design**

Class: BSE[4]-3(A/B)

Course Instructor: **DR. SYED SAMAR YAZDANI**

Submission Date:

COURSE CODE: CEN 220

Shift:

Time Allowed:

Max. Marks: **10 Marks**

A combinational circuit has four inputs and one output. The output is equal to 1 when (1) all the inputs are equal to 1 when

- (1) all the inputs are equal to 1 or
- (2) none of the inputs are equal to 1 or
- (3) an odd number of inputs are equal to 1

- (a) Obtain the truth table.
- (b) Find the simplified output function in sum of products
- (c) Find the simplified output function in product of sums