



BAHRIA UNIVERSITY, (Karachi Campus)

Department of Software Engineering

QUIZ - 2

COURSE TITLE: **Computer Architecture & Logic Design**

Class: BSE[4]-3(A/B)

Course Instructor: **DR. SYED SAMAR YAZDANI**

Submission Date:

COURSE CODE: CEN 220

Shift:

Time Allowed:

Max. Marks: **10 Marks**

2-bit Adder

K-map for X

CD \ AB	A		B
	0	1	
C	0	0	0
	1	0	1

K-map for Y

CD \ AB	A		B
	0	1	
C	0	0	1
	1	1	0

K-map for Z

CD \ AB	A		B
	0	1	
C	0	1	0
	1	0	1

X =

Y =

Z =