

Truth Table to Boolean Expression

❖ Read off of table

- For 1, write variable name
- For 0, write complement of variable

a	b	c
0	0	0
0	1	1
1	0	1
1	1	0

❖ *Sum of Products (SoP)*

- Take rows with 1's in output column, sum products of inputs
- $C = \bar{A}B + \bar{B}A$

❖ *Product of Sums (PoS)*

- Take rows with 0's in output column, product the sum of the *complements of the inputs*
- $C = (A + B) \cdot (\bar{A} + \bar{B})$

We can show that these are equivalent!

Basic Boolean Identities

$$\diamond X + 0 = X$$

$$\diamond X \cdot 1 = X$$

$$\diamond X + 1 = 1$$

$$\diamond X \cdot 0 = 0$$

$$\diamond X + X = X$$

$$\diamond X \cdot X = X$$

$$\diamond X + \overline{X} = 1$$

$$\diamond X \cdot \overline{X} = 0$$

$$\diamond \overline{\overline{X}} = X$$

Basic Boolean Algebra Laws

- ❖ Commutative Law:

$$X + Y = Y + X$$

$$X \cdot Y = Y \cdot X$$

- ❖ Associative Law:

$$X + (Y + Z) = (X + Y) + Z$$

$$X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$$

- ❖ Distributive Law:

$$X \cdot (Y + Z) = X \cdot Y + X \cdot Z$$

$$X + YZ = (X + Y) \cdot (X + Z)$$

Advanced Laws (Absorption)

$$\diamond X + XY = X$$

$$\diamond XY + X\bar{Y} = X$$

$$\diamond X + \bar{X}Y = X + Y$$

$$\diamond X(X + Y) = X$$

$$\diamond (X + Y)(X + \bar{Y}) = X$$

$$\diamond X(\bar{X} + Y) = XY$$

Practice Problem

❖ Boolean Function: $F = \bar{X}YZ + XZ$

Truth Table:

X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Simplification:

Lecture Outline

- ❖ Course Logistics
- ❖ Course Motivation
- ❖ Combinational Logic Review
- ❖ **Combinational Logic in the Lab**

Why Is This Useful?

- ❖ Logic minimization: reduce complexity at gate level
 - Allows us to build smaller and faster hardware
 - Care about both # of gates, # of literals (gate inputs), # of gate levels, and types of logic gates

Why Is This Useful?

❖ Faster hardware?

- Fewer inputs implies faster gates in some technologies
- Fan-ins (# of gate inputs) are limited in some technologies
- Fewer levels of gates implies reduced signal propagation delays
- # of gates (or gate packages) influences manufacturing costs
- Simpler Boolean expressions → smaller transistor networks → smaller circuit delays → faster hardware
- Does the type of gate matter?

Does the Type of Gate Matter?

❖ Yes!

2-Input Gate Type	# of transistors
NOT	2
AND	6
OR	6
NAND	4
NOR	4
XOR	8
XNOR	8

- ❖ Can recreate all other gates using only NAND or only NOR gates
 - Called “universal” gates
 - *e.g.* $A \text{ NAND } A = \bar{A}$, $B \text{ NOR } B = \bar{B}$
 - DeMorgan’s Law helps us here!

DeMorgan's Law

$$\diamond \overline{X + Y} = \bar{X} \cdot \bar{Y}$$

$$\diamond \overline{X \cdot Y} = \bar{X} + \bar{Y}$$

X	Y	\bar{X}	\bar{Y}	NOR		NAND	
				$\overline{X + Y}$	$\bar{X} \cdot \bar{Y}$	$\overline{X \cdot Y}$	$\bar{X} + \bar{Y}$
0	0	1	1	1		1	
0	1	1	0	0		1	
1	0	0	1	0		1	
1	1	0	0	0		0	


- ❖ In Boolean Algebra, converts between NAND/NOR and OR/AND expressions

- $Z = \overline{(A + B + \bar{C}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C})}$

- $Z = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$


- At gate level, can convert from NAND/NOR to OR/AND gates

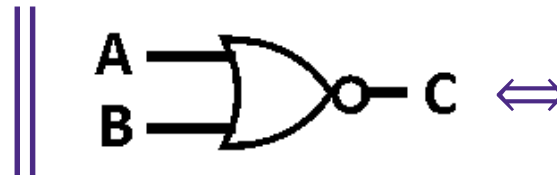- “Flip” all input/output bubbles and “switch” gate




DeMorgan's Law Practice Problem

- ❖ Simplify the following diagram:

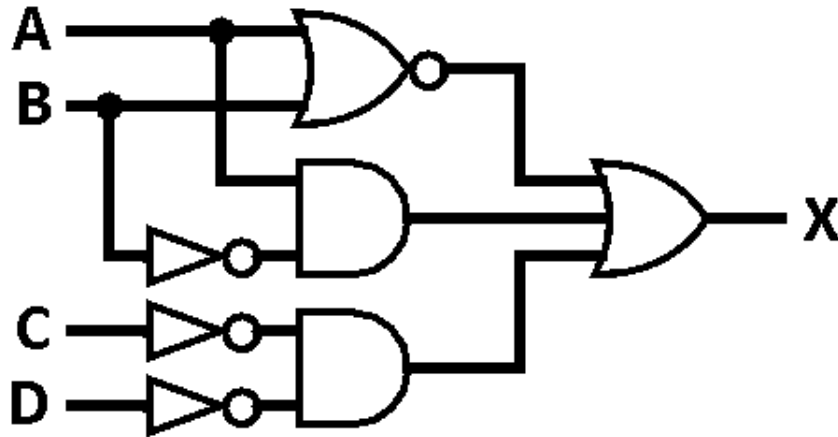

- ❖ Then implement with only NAND gates:

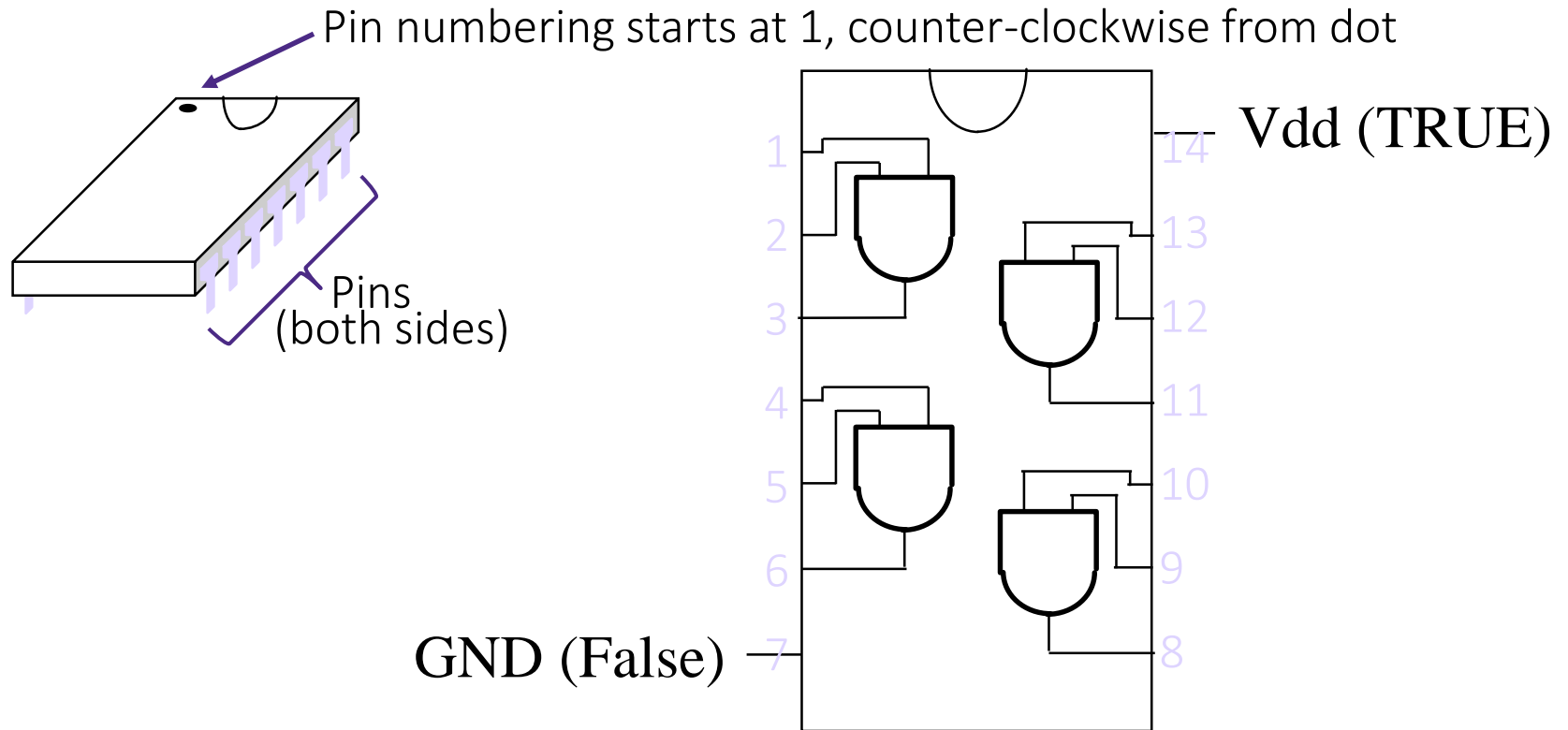
Transistor-Transistor Logic (TTL) Packages



- ❖ Diagrams like these and other useful/helpful information can be found on part **data sheets**
 - It's really useful to learn how to read these


Mapping truth tables to logic gates

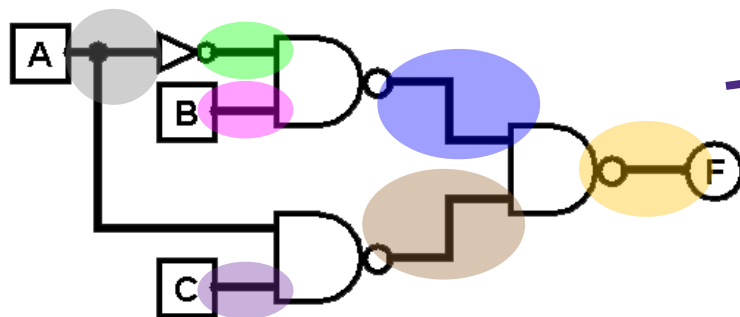- ❖ Given a truth table:
 - 1) Write the Boolean expression
 - 2) Minimize the Boolean expression
 - 3) Draw circuit diagram with gates
 - 4) Map to available gates
 - 5) Determine # of packages and their connections





7 nets (wires) in this design

(4) →

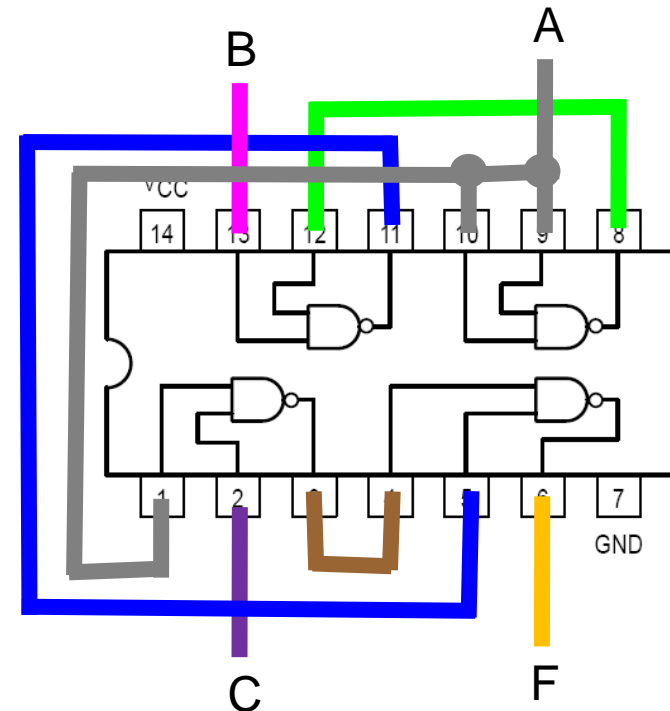

Breadboarding circuits

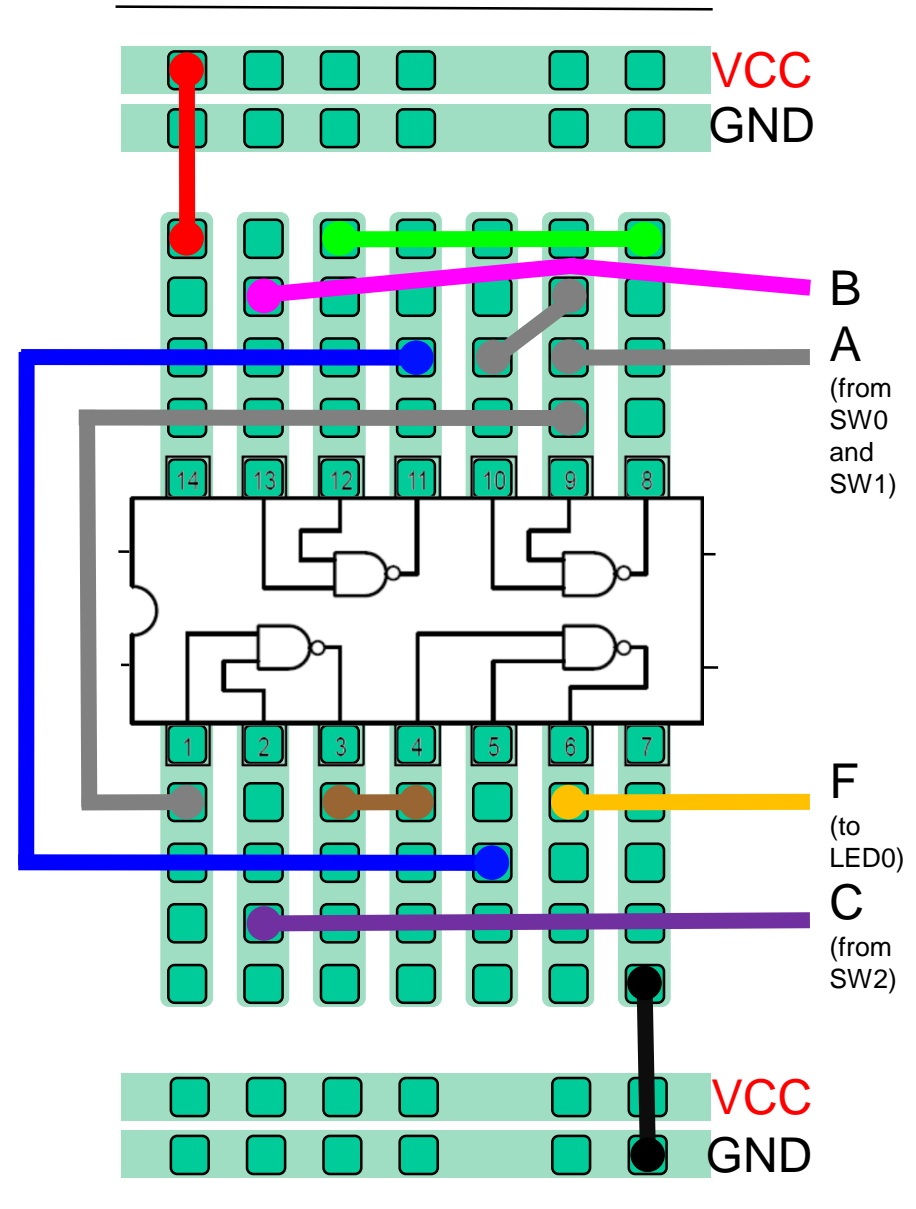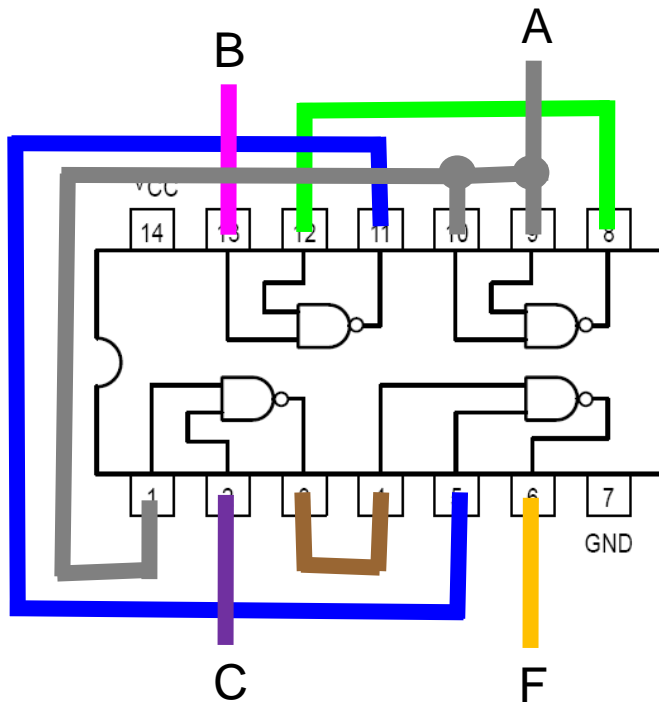

Summary

- ❖ Digital systems are constructed from Combinational and Sequential Logic
- ❖ Logic minimization to create smaller and faster hardware
- ❖ Gates come in TTL packages that require careful wiring

