

Practice Problem

- ❖ Boolean Function: $F = \bar{X}YZ + XZ$

Truth Table:

X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Simplification:

=

28

Why Is This Useful?

- ❖ Logic minimization: reduce complexity at gate level
 - Allows us to build smaller and faster hardware
 - Care about both # of gates, # of literals (gate inputs), # of gate levels, and types of logic gates

31

DeMorgan's Law

- ❖ $\overline{X + Y} = \bar{X} \cdot \bar{Y}$

- ❖ $\overline{X \cdot Y} = \bar{X} + \bar{Y}$

X	Y	\bar{X}	\bar{Y}	$\overline{X + Y}$ (NOR)	$\overline{X \cdot Y}$ (NAND)
0	0	1	1	1	1
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	0

- ❖ In Boolean Algebra, converts between AND-OR and OR-AND expressions

- $Z = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$

- $\bar{Z} = (A + B + \bar{C}) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C})$

- ❖ At gate level, can convert from AND/OR to NAND/NOR gates


- "Flip" all input/output bubbles and "switch" gate



34

DeMorgan's Law Practice Problem

- ❖ Simplify the following diagram:

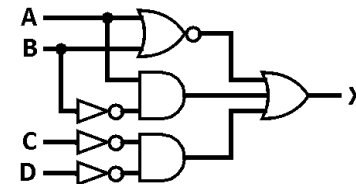

- ❖ Then implement with only NAND gates:

35